



Sequential Circuits, Bus

Online Ch 20.1-3 [Sta10]

Circuits with memory

Flip-Flop

S-R Latch

Registers, Counters

Ch 3 [Sta10]

What moves on Bus?



Bus characteristics


PCI-bus




Flip-Flop (*kiikku*)

 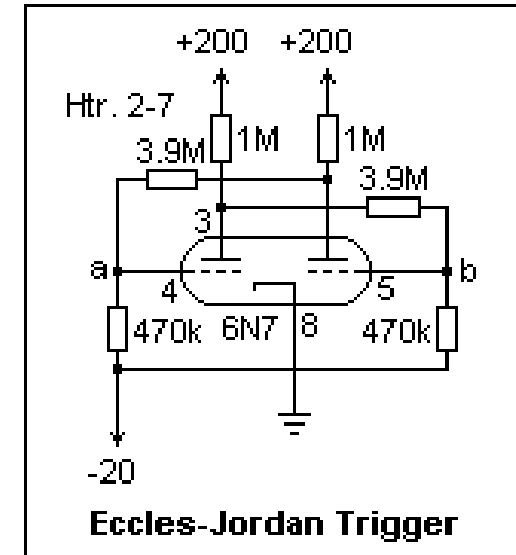- William Eccles & F.W. Jordan
 - with vacuum tubes, 1919
- 2 states for Q (0 or 1, true or false)
 - 1-bit memory
 - **Maintains state when input absent**
- 2 outputs
 - complement values
 - both always available on different pins
- Need to be able to change the state (Q)



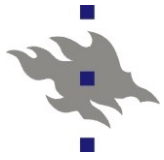

S-R Flip-Flop or S-R Latch (*salpa*)

 


S = “SET” = “Write 1” = “set S=1 for a short time”

R = “RESET” = “Write 0” = “set R=1 for a short time”

Use NOR gates

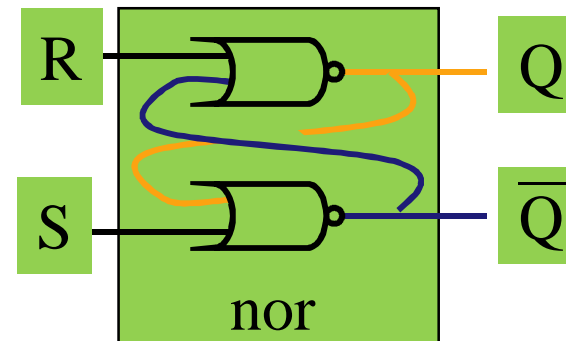$\text{nor}(0, 0) = 1$
 $\text{nor}(0, 1) = 0$
 $\text{nor}(1, 0) = 0$
 $\text{nor}(1, 1) = 0$






Clocked Flip-Flops

- State change can only when clock is 1
 - more control on state changes


- Clocked S-R Flip-Flop

- D Flip-Flop
 - only one input D
 - D = 1 and CLOCK → write 1
 - D = 0 and CLOCK → write 0

- J-K Flip-Flop
 - Toggle Q when J=K=1

 

(Sta10 Fig 20.24)

 

Basic Clocked Flip-flops

Name	Graphic Symbol	Characteristic Table															
S-R		<table border="1"> <thead> <tr> <th>S</th> <th>R</th> <th>Q_{n+1}</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>Q_n</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>-</td> </tr> </tbody> </table>	S	R	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	-
S	R	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	-															
J-K		<table border="1"> <thead> <tr> <th>J</th> <th>K</th> <th>Q_{n+1}</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>Q_n</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>$\overline{Q_n}$</td> </tr> </tbody> </table>	J	K	Q_{n+1}	0	0	Q_n	0	1	0	1	0	1	1	1	$\overline{Q_n}$
J	K	Q_{n+1}															
0	0	Q_n															
0	1	0															
1	0	1															
1	1	$\overline{Q_n}$															
D		<table border="1"> <thead> <tr> <th>D</th> <th>Q_{n+1}</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> </tr> </tbody> </table>	D	Q_{n+1}	0	0	1	1									
D	Q_{n+1}																
0	0																
1	1																

(not Q_n)



Registers

Parallel registers

- read/write
- CPU user registers
- additional internal registers

Shift Registers

- shifts data 1 bit to the right
- serial to parallel?
- ALU ops?
- rotate?



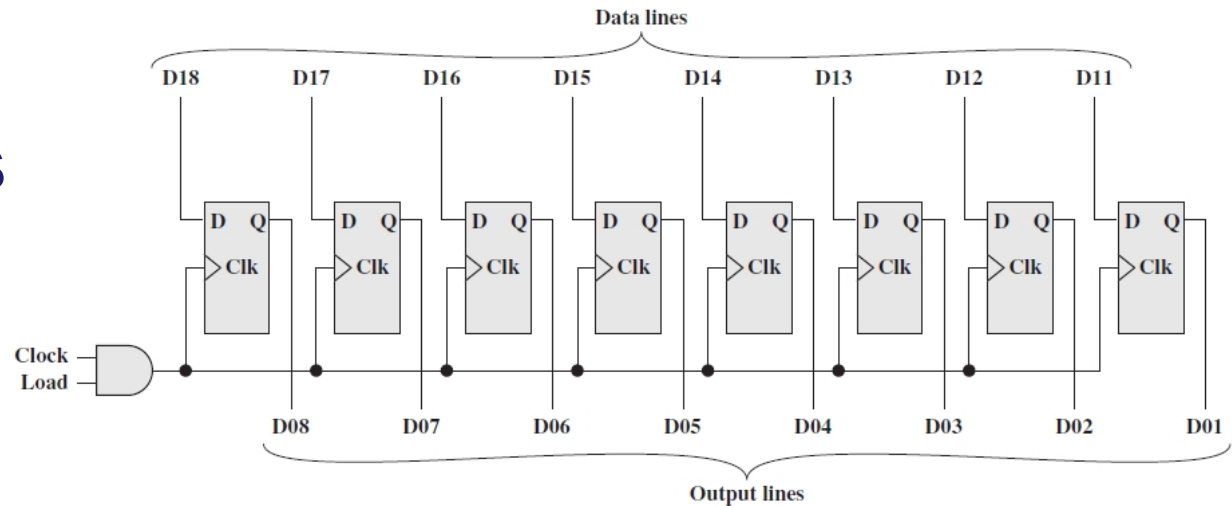


Figure 20.28 8-Bit Parallel Register

 


Sta10 Fig 20.29

 


Counters

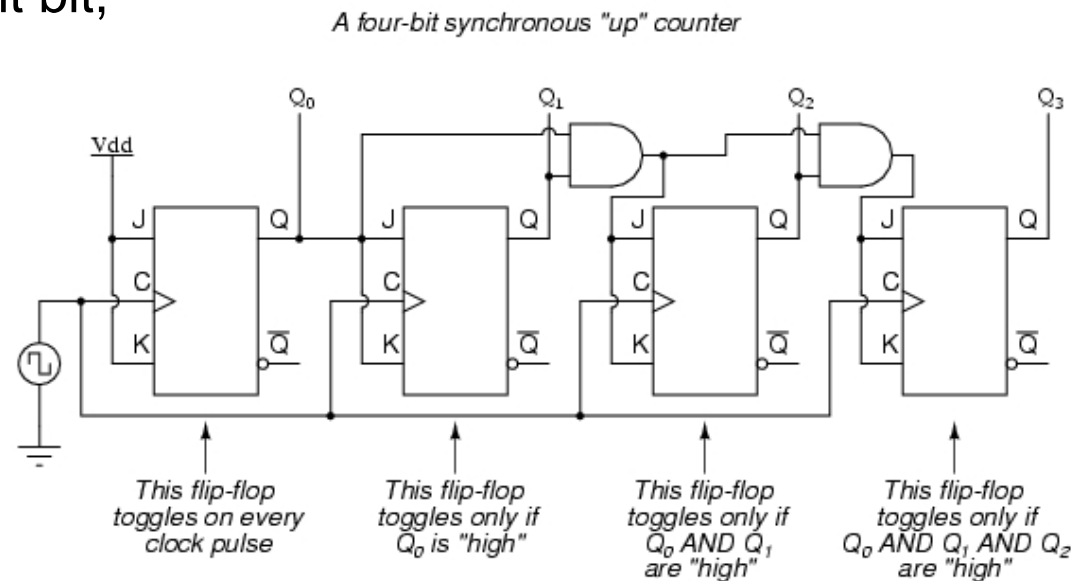- Add 1 to stored counter value
- Counter
 - parallel register plus increment circuits
- Ripple counter (aalto, viive)
 - asynchronous
 - increment least significant bit,
 - and handle “carry” bit as far as needed
- Synchronous counter
 - modify all counter flip-flops simultaneously
 - faster, more complex, more expensive



space-time tradeoff

(<http://www.allaboutcircuits.com>)

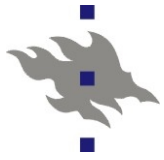

Digital Logic Summary

- Boolean algebra
- Gates – not, nand, xor, and, or
- Circuits
 - Presentation: Boolean equations, Truth tables, Graphical Symbols
 - Simplification with Karnaugh Maps
- Combination Circuits – output depends on input only
 - Set inputs, wait, output ready – no dynamic state memory
 - ROM
- Sequential Circuits – output depends also on internal state
 - Flip-Flops, registers, counters, memory
- Implement Computer
 - apply combination and sequential circuits smartly

Discussion?



HELSINGIN YLIOPISTO
HELSINGFORS UNIVERSITET
UNIVERSITY OF HELSINKI


Bus (Väylä)


Ch 3 [Sta10]

What moves on Bus?

Bus characteristics


PCI -bus

 

 

Bus

(Sta10 Fig 3.16)

 

- For communication with and between devices
- Broadcast (*yleislähetys*) - most common
 - Everybody hear everything
 - React to messages/signals to itself only
- Each device has its own control and status information
 - Device driver (OS) moves control data to device controller's registers
 - ~ memory address, device address, how much, direction
 - Device driver reads the status from the controller's status register
 - Ready? Operation successful? ...



Bus structure

- Control lines (*Ohjausväylä, ~ johtimet*)
 - Control and timing information
 - Operations: like memory read, memory write, I/O read
 - Interrupt request
 - Clock
- Address lines (*Osoiteväylä*)
 - Source and destination ids
 - Memory address, device address (module, port)
 - For transfer source and destination
 - Width (number of parallel lines) determines directly addressable memory address space (*osoiteavaruuden koko*)
 - For example: 32 b \Rightarrow 4 GB




Bus structure

- Data lines (*dataväylä*)
 - All processing information:
 - Instructions
 - Data
 - DMA-transfer contents
 - Width determines the maximum number of bits that can be transferred at the same time
 - For example 38b wide line allows 32 bits data plus 6 Hamming-coded parity bits



What moves on the bus?

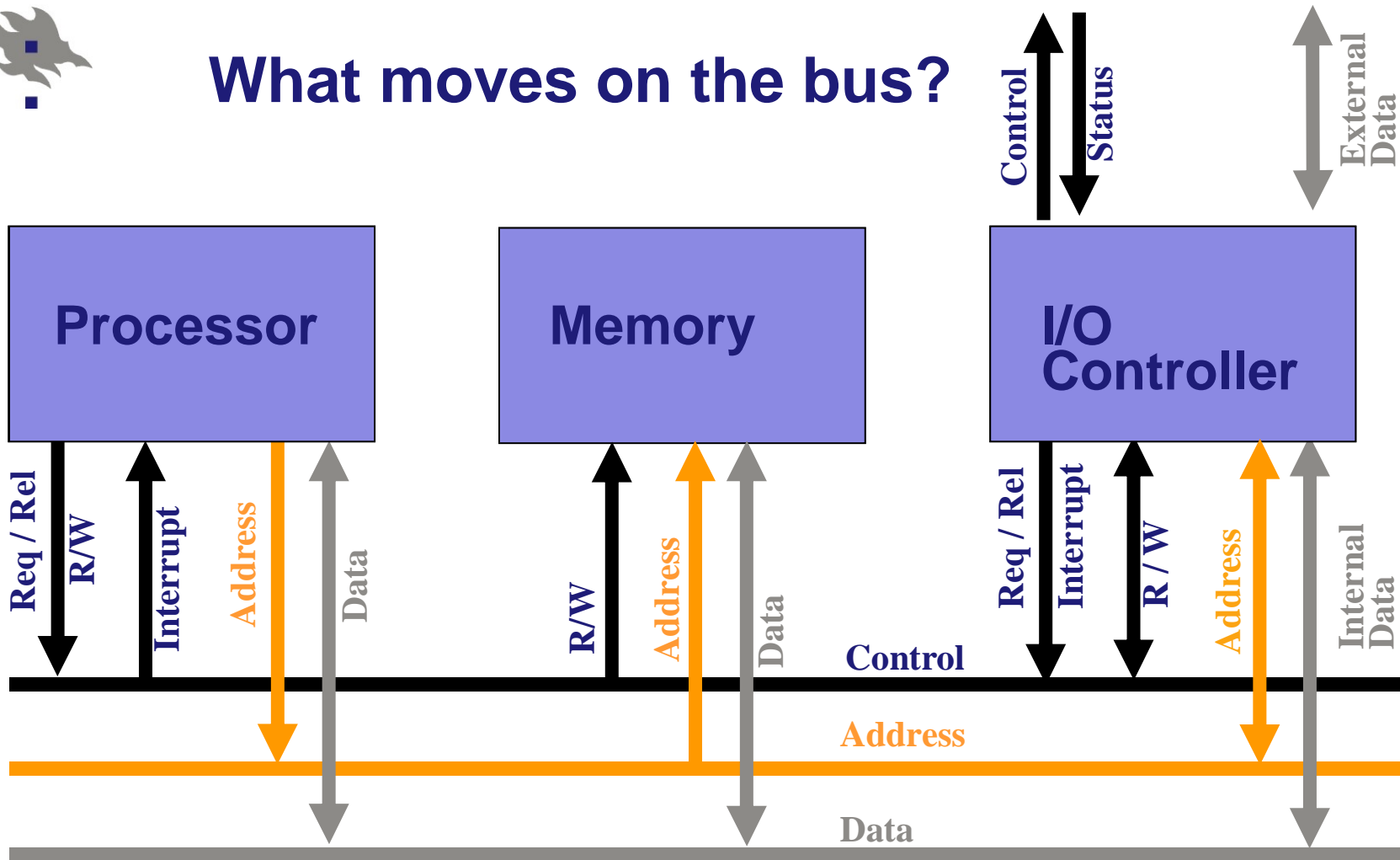


- **Timing**

- **Memory-mapped I/O**

- **DMA**




Bus = Bottleneck?

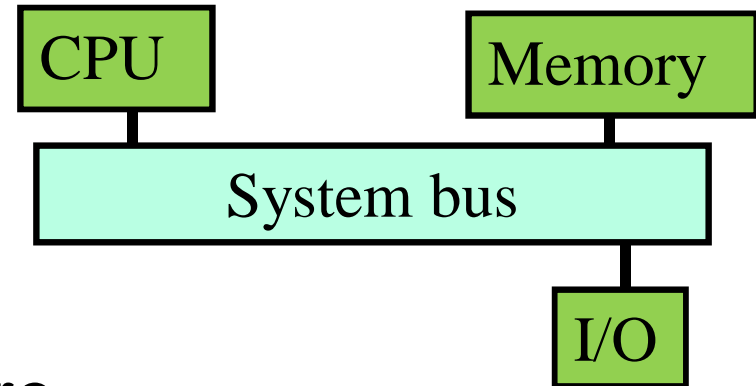

■ von Neumann architecture

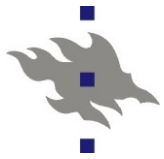- Instructions and data both in main memory
- All memory content referred using address
- Sequentially ordered instructions executed sequentially
 - unless order changed explicitly (jumps, branches)



Bus characteristics

Width


- ~ 50 – 100 lines (*johdin*)
- mother board, cable, connectors

Bus type

- Dedicated, non-multiplexed (*dedikoitu*)
 - Address and data – separate lines
- Time multiplexed (*aikavuorottelu*)
 - Address and data share lines
 - Address valid / data valid -line

Arbitration (*vuoron varaus*)

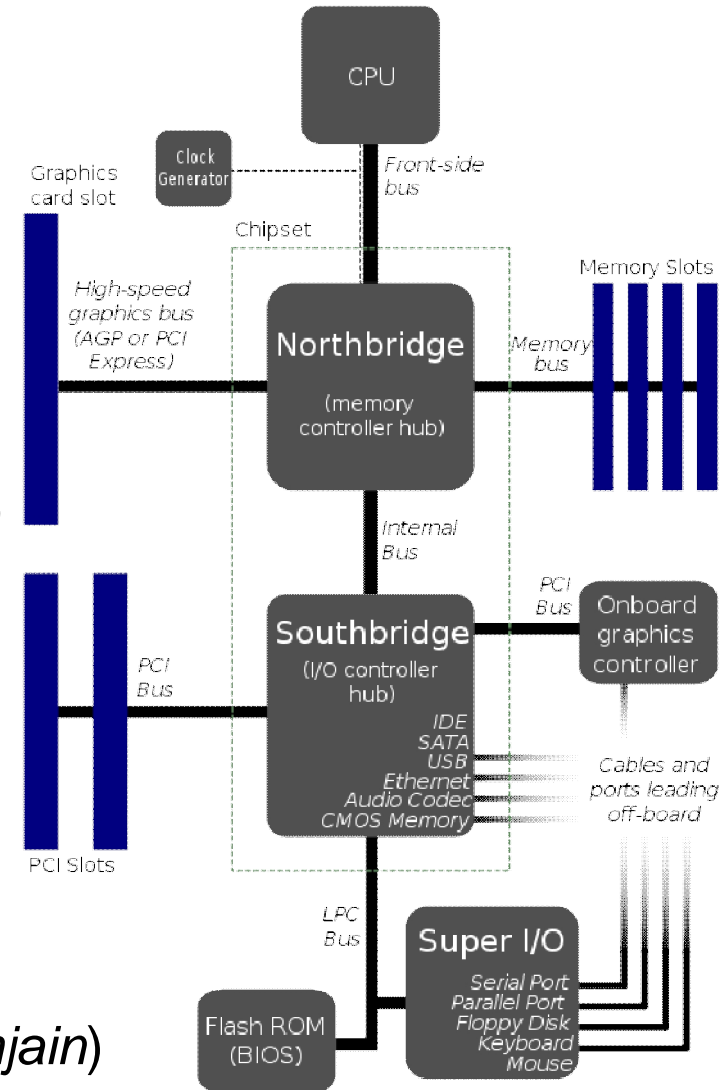- Centralized
 - One bus controller, arbiter (*väyläohjain*)
- Distributed
 - Controllers have necessary logic



<http://en.wikipedia.org/wiki/Motherboard>



Bus characteristics

■ Timing (*ajoitus, tahdistus*)

■ Synchronous (*tahdistettu*)

- Regular clock cycle (*kellopulssi*) – sequence of 0s and 1s

■ Asynchronous

- Separate signals when needed

■ Shared traffic rules

- everyone knows what is going to happen next

■ Efficiency (*tehokkuus*)

■ Bandwidth (*kaistanleveys*)

- How many bits per second



Synchronous timing

- Based on clock
 - Control line has clock pulse (cycle 1-0)
 - All devices "hear" the same pulse
- Event takes one cycle (commonly)
 - Start at the begin of the cycle (leading edge)
 - For example, reading data takes one cycle
- All devices in the bus work at the same pace
 - Slowest determines the speed of all
 - Each device knows the speed of the others
 - Each device knows, when the other is ready for next event
- "Do this during the next cycle"
 - Device can count on the other one to do it!




Asynchronous timing

- Devices can use arbitrary speeds (variation allowed)
 - Processing time depends on the device
 - Device can determine, when the other one is ready
 - How long is the event going to last to perform?
- Synchronization using a special signal
 - Send synchronization signal, when work done and ready
 - Address and data on bus \Rightarrow send signal "write"
(for example: change "write"-line to 1)
 - Data stored to memory \Rightarrow send signal "ack"
 - Time of the next event depends on signals
- "Do this when you have time, inform me when ready"
 - Wait until get signal that "this" is done




Timing diagrams (*ajoituskaavio*)

- See Appendix 3a [Sta10, Ch 3]

 


(a) Signal as a function of time

“assert” or
“active”
= 0-level

 

(b) Groups of lines

 

Response or Response#

(c) Cause-and-effect dependencies


(Sta10 Fig 3.27)

Asserted on 0; asserted on 1

Synchronous Timing




Initiator CPU
(for example)

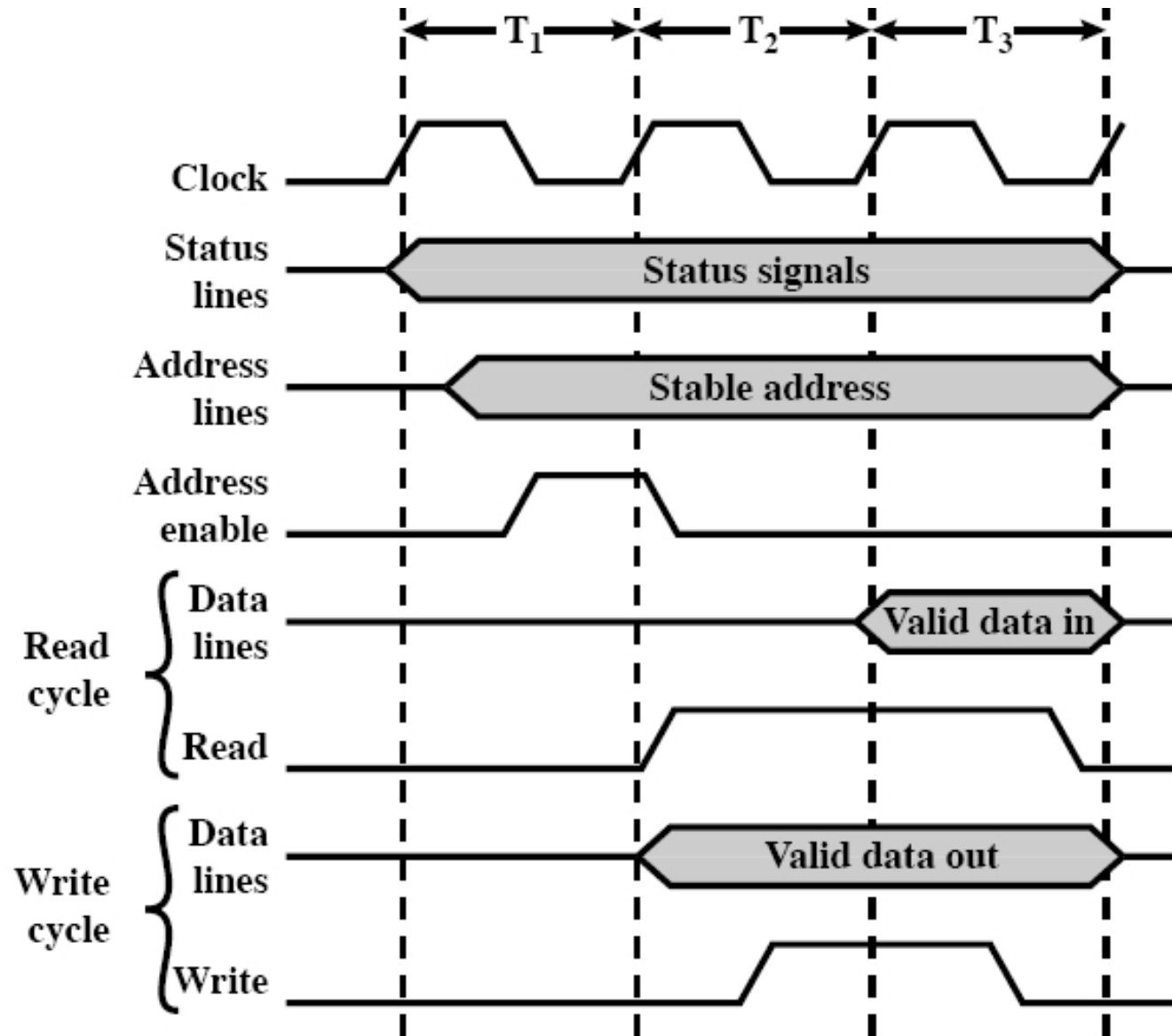

(Sta10 Fig 3.19)




Asynchronous timing - Read

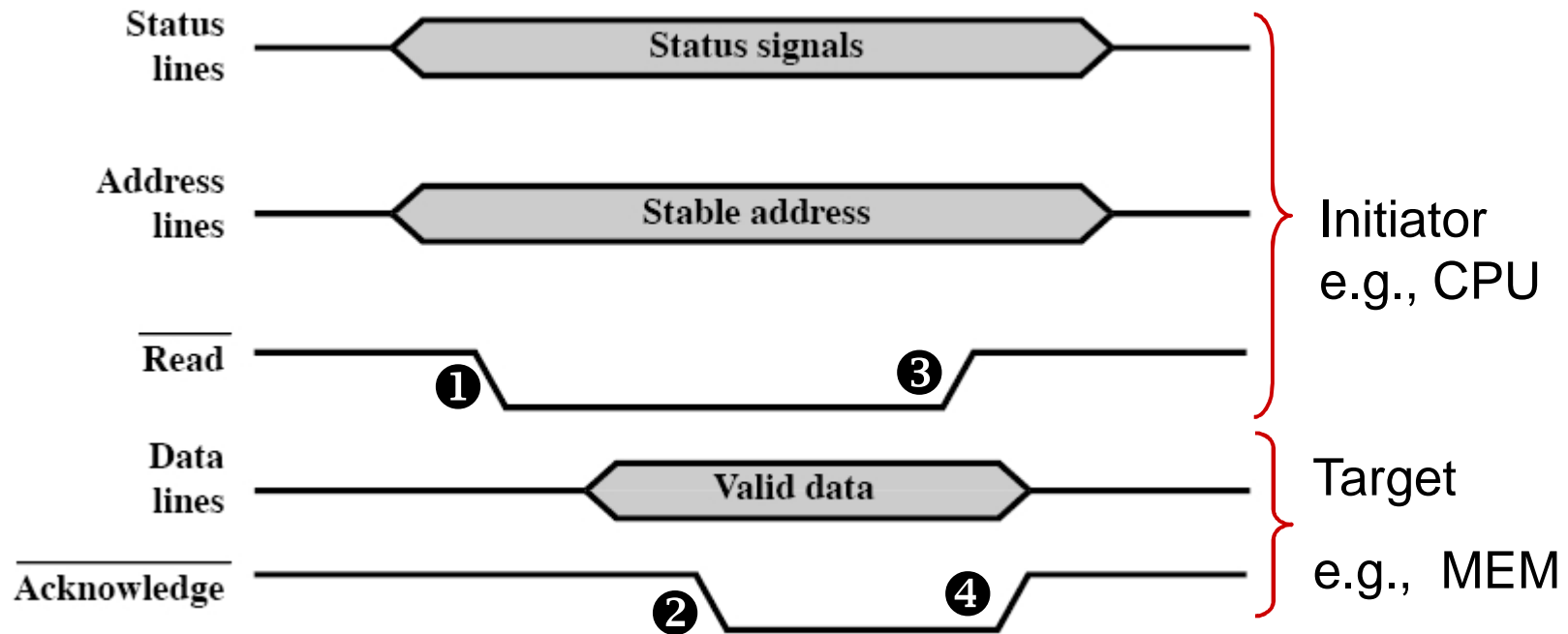

(Sta10 Fig 3.20a)




Asynchronous timing - Write

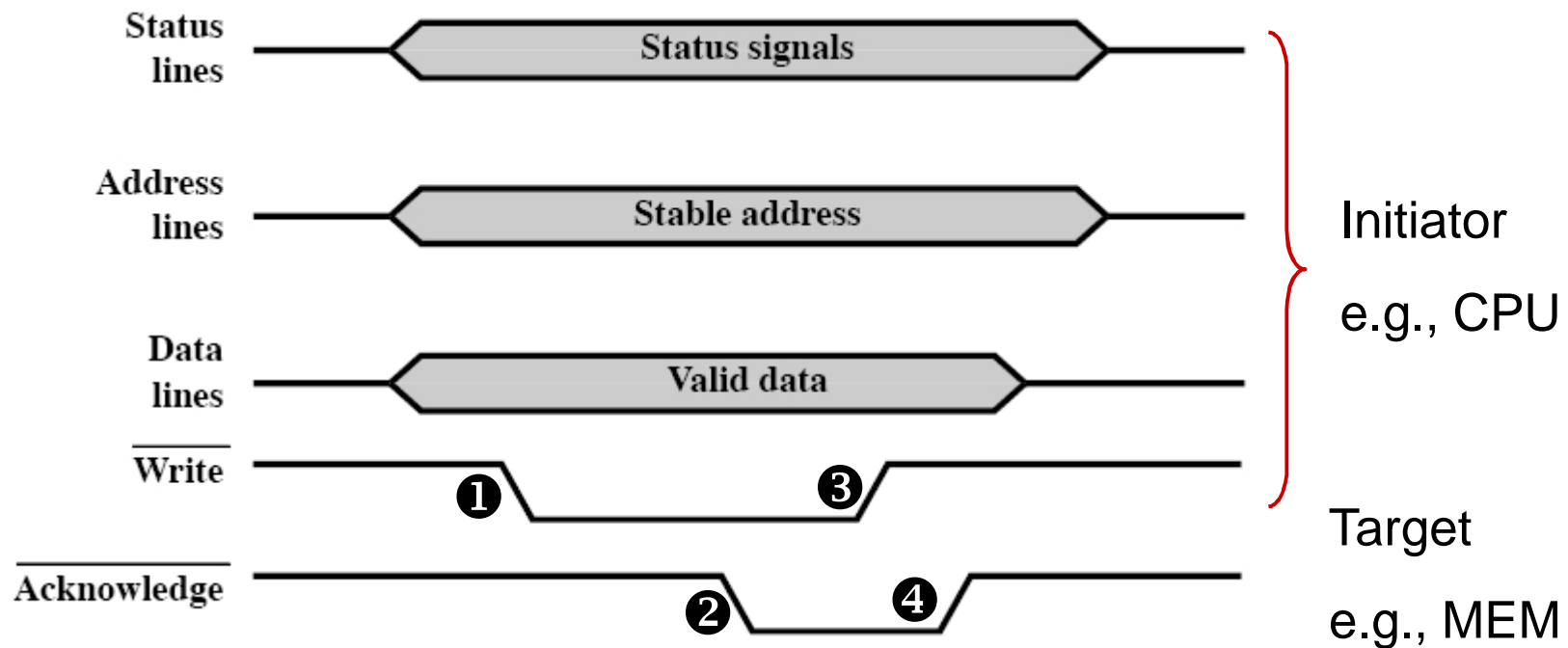


(Sta10 Fig 3.20b)


Discussion?

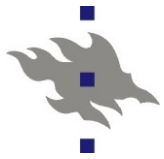

Bus Events (*väylätapahtumia*)

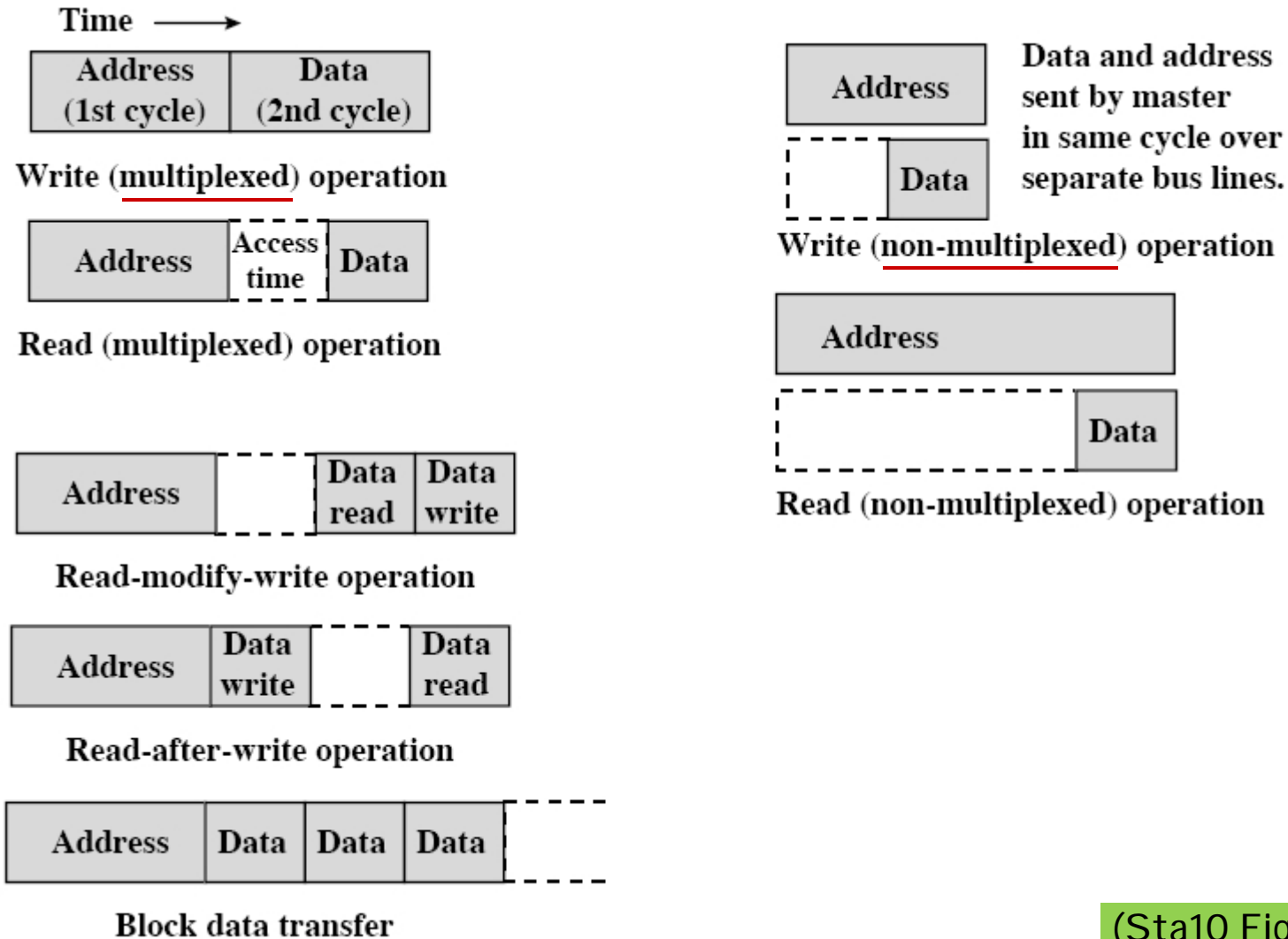


(Sta10 Fig 3.21)

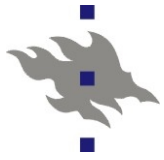

Bus Configuration


- All devices on one bus?
 - All must use the same technique
 - Long bus \Rightarrow large propagation delay (*etenemisviive*)
 - Combined data rates of the devices may exceed the capacity of the bus
 - Collisions on the arbitration, extra wait
 - Synchronous? \Rightarrow slowest determines the speed of all
- Bus hierarchy
 - Isolate independent traffic from each other
 - Maximize the most important transfer pace
CPU \Leftrightarrow MEM
 - I/O can manage with lower speed

 


Bottleneck!



Bus Hierarchy Typical Pentium 4

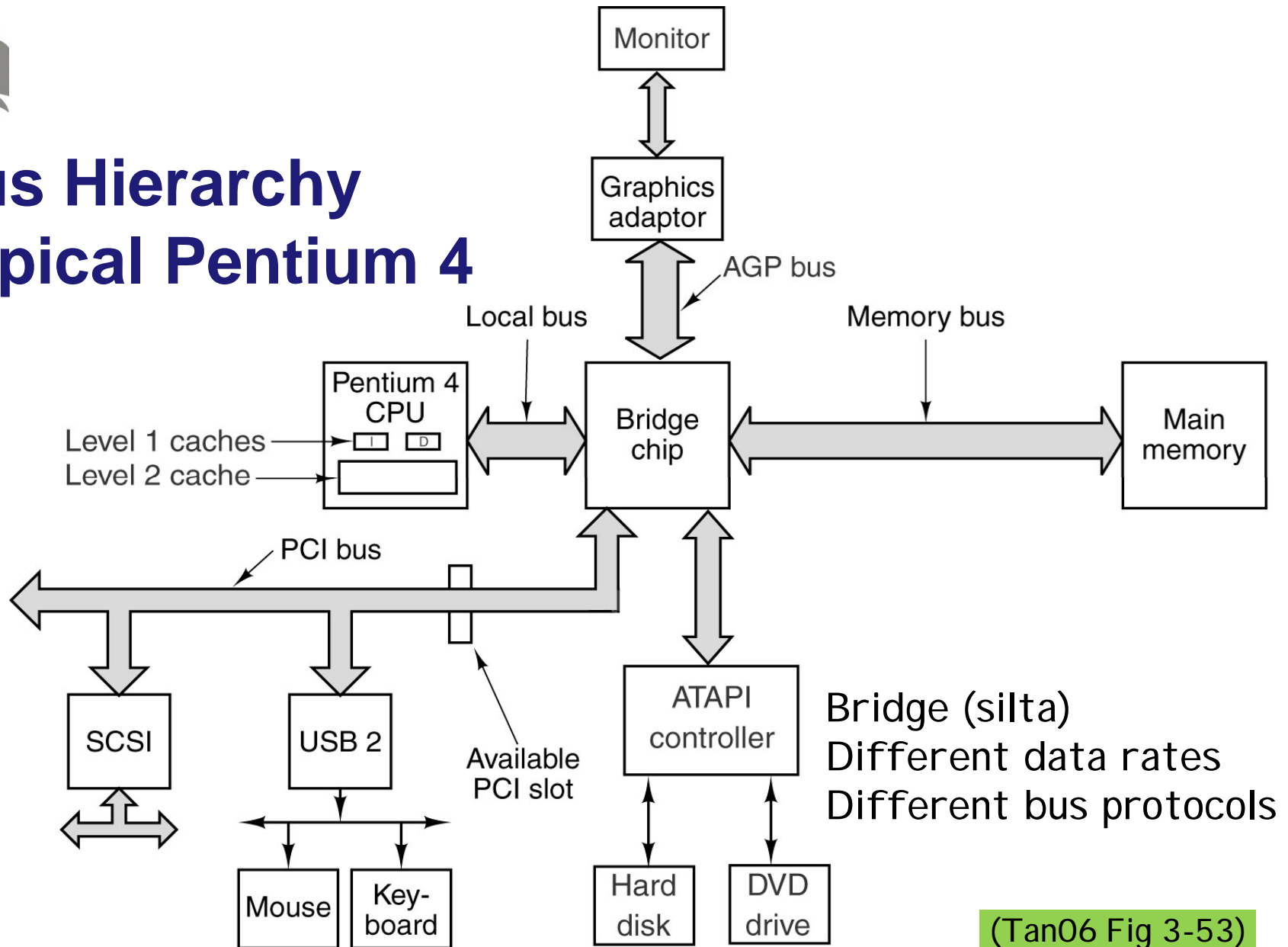

(Tan06 Fig 3-53)

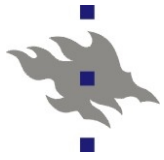


Computer Organization II

PCI-bus


[Sta10, Ch 3.5]
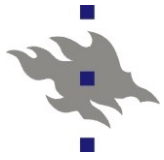
<http://www.soe.ucsc.edu/classes/cmpe003/Spring02/motherboard.gif>



PCI: Peripheral Component Interconnect

- 49 mandatory (+51 optional) signal lines
 - Address data: 32b mandatory (optional allows 64b)
 - Other signals: 17 mandatory (+ 19 optional)
- Centralized arbiter (*keskitetty väylän varaus*)
- Synchronous timing (*synkroninen tahdistus*)
 - own 33 or 66 MHz clock (PCI-X: 133/156/533 Mhz)
 - Transfer rate 133, 266, 532 MB/s (PCI-X: 1 GB/s,4 GB/s)
- Events on the bus
 - read, write, read block, write block (multiplexed)
- Max 16 devices

 

49 Mandatory Signal Lines (PCI)

(Sta10 Table 3.3)

- AD[32]: address or data, multiplexed (*aikavuorottelu*)
 - + 1 parity
- C/BE[4]: bus command tai byte enable, multiplexed
 - For example: 0110/1111 = memory read/all 4 Bytes
- CLK, RST#: clock, reset
- 6 for interface control
 - FRAME#, IRDY#, TRDY#, STOP#, IDSEL, DEVSEL#
- 2 for arbitration (*väylän varaus*)
 - REQ# requires, GNT# granted
 - Dedicated lines for devices
- 2 error reporting pins (lines)
 - PERR# parity, SERR# system





51 Optional Signal Lines (PCI)

(Sta10 Table 3.4)


- 4 lines for interrupt requests (*keskeytyspyyntö*)
 - Each device has its own dedicated line(s)
- 2 lines for cache support (on CPU or other devices)
 - snoop cache
- 32 A/D extra lines
 - 32 mandatory + 32 optional => 64 bit address/data lines
- 4 additional lines for C/BE bus command/byte enable
- 2 lines to negotiate 64b transfer
- 1 extra parity line
- 5 lines for testing




PCI Transactions

(Sta10 Fig 3.24)

 - Bus activity as transactions
 - New bus request for each new transaction
- (1) Bus reservation
 - Central arbiter
 - send REQ, wait for GNT
- (2) Bus transaction
 - Initiator or master (device who reserved the bus)
 - Begin by asserting FRAME (reserve of bus)
 - Stop by releasing FRAME (indicate free bus)



Bus arbitration : A and B want bus

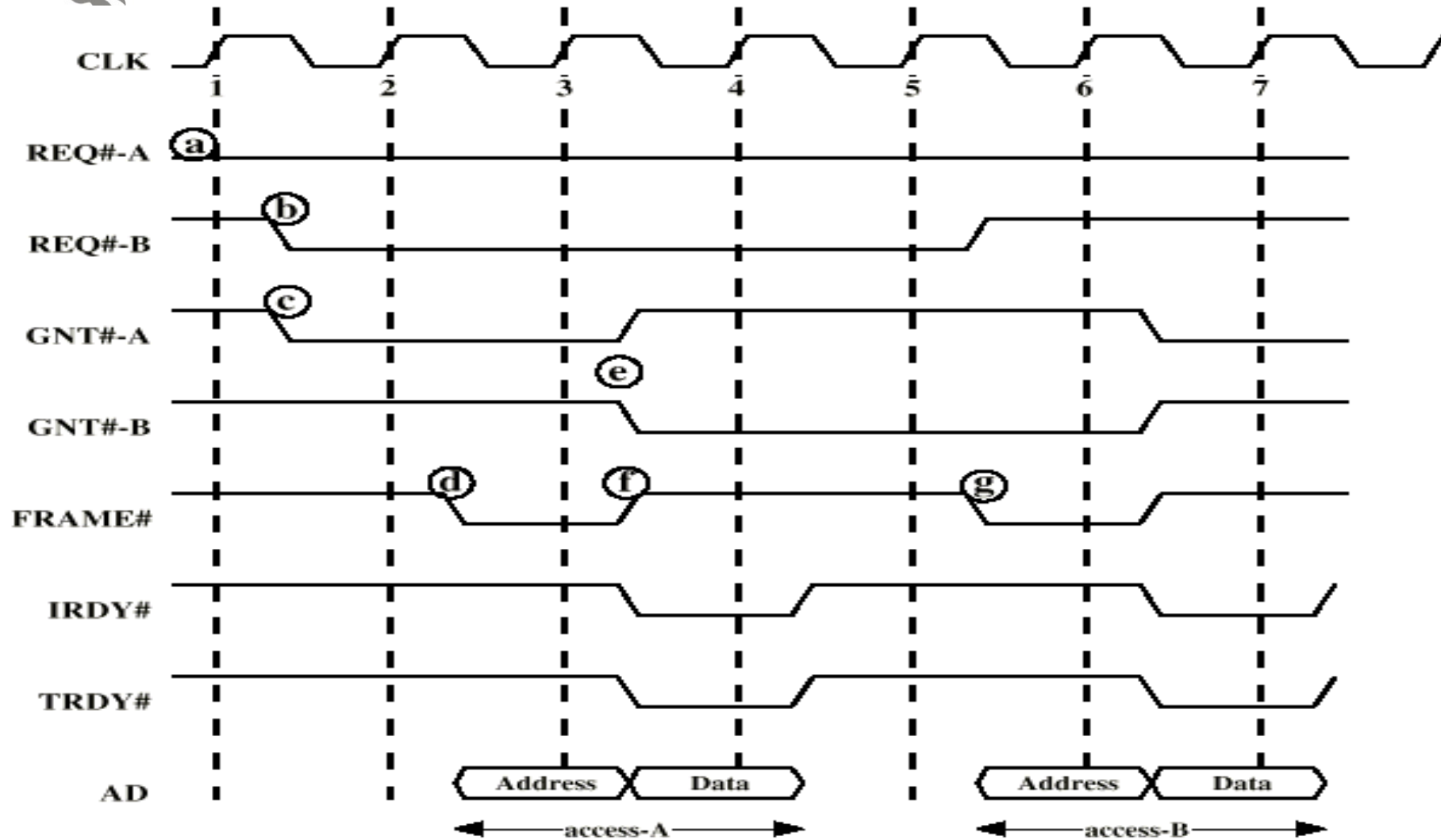

(Sta10 Fig 3.25)

a) A wants bus

b) B wants bus

c) A granted bus

d) A starts frame, requests also for next transaction

e) Grants bus to for next trans.

g) B starts frame, no more B req.

A knows that it has bus and bus is available

Sees that both still want it

f) A marks last frame transfer, marks data ready


A's target reads data

Sees that only A wants it

A action

B action


Arbiter action

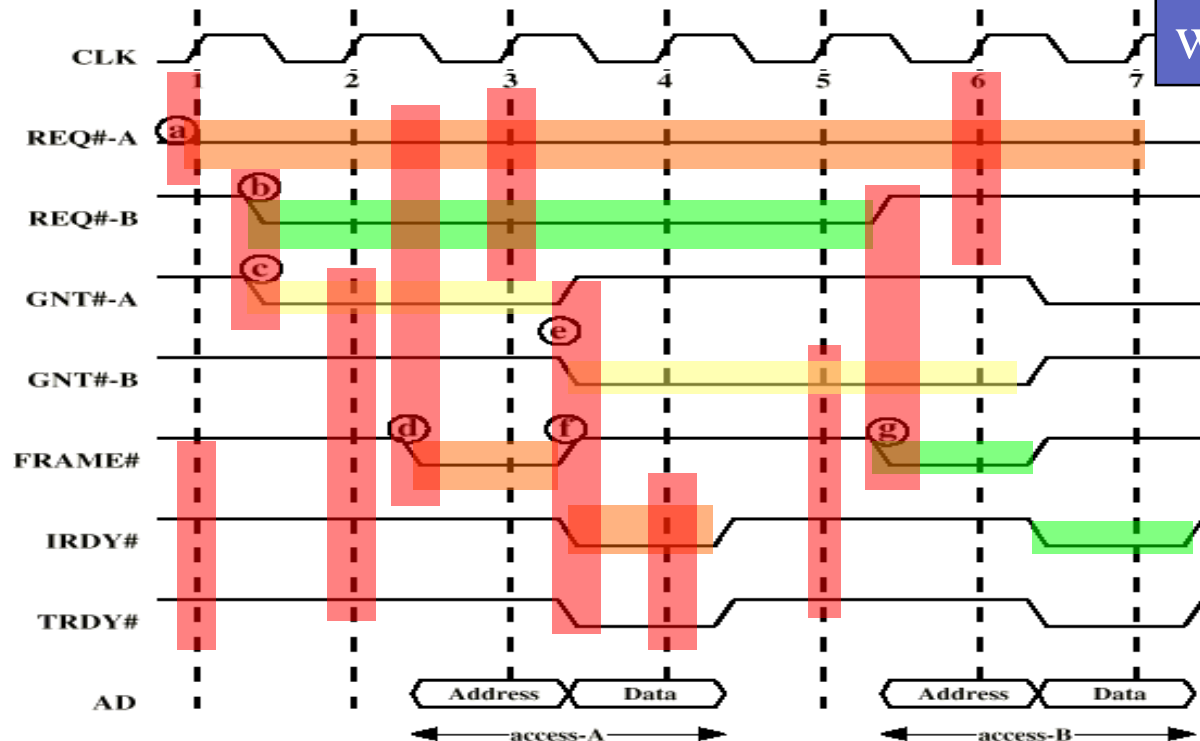


All ready for new trans

All ready for new trans, granted for B, B knows that it has bus

PCI Memory Read

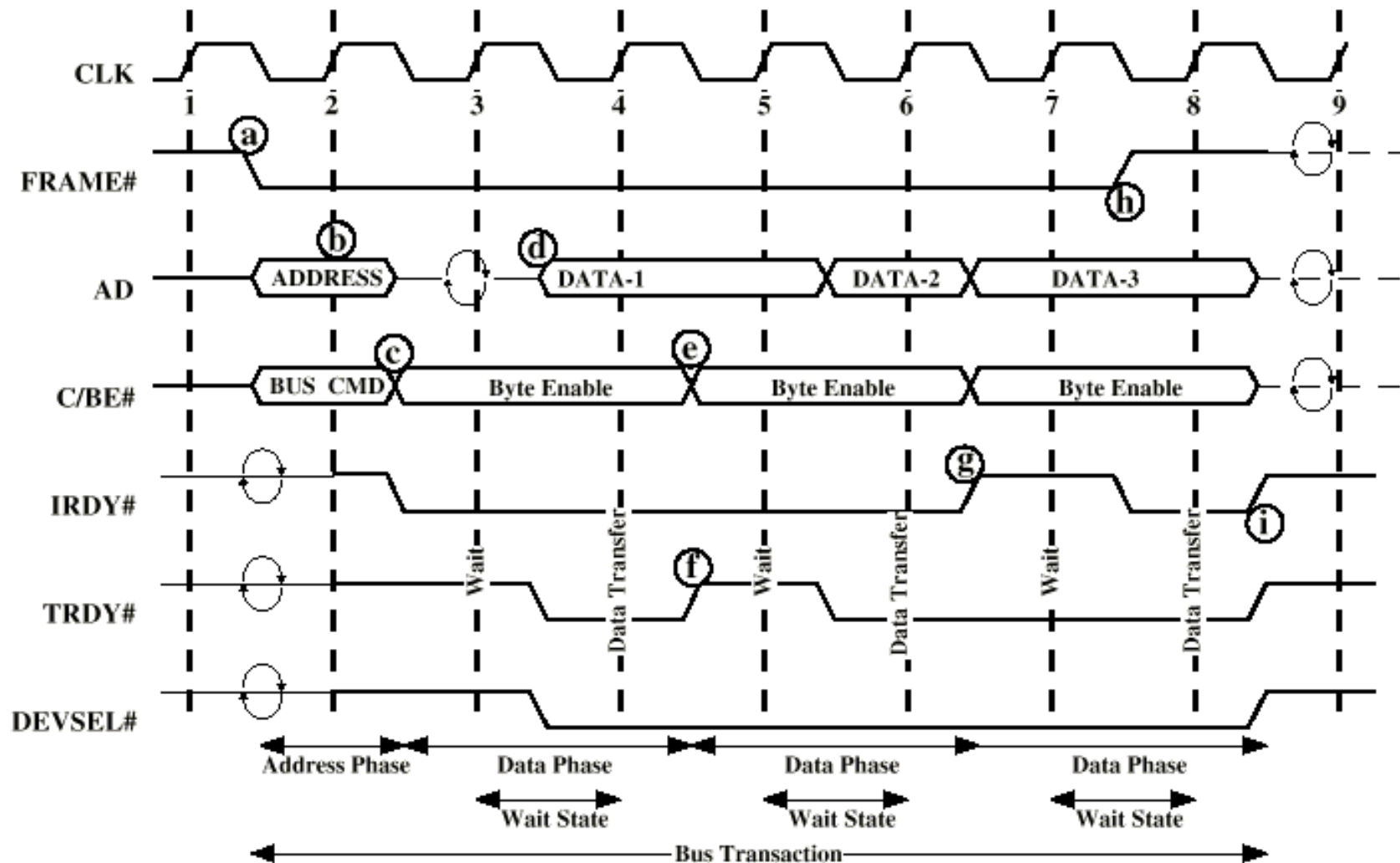


(Sta10 Fig 3.23)

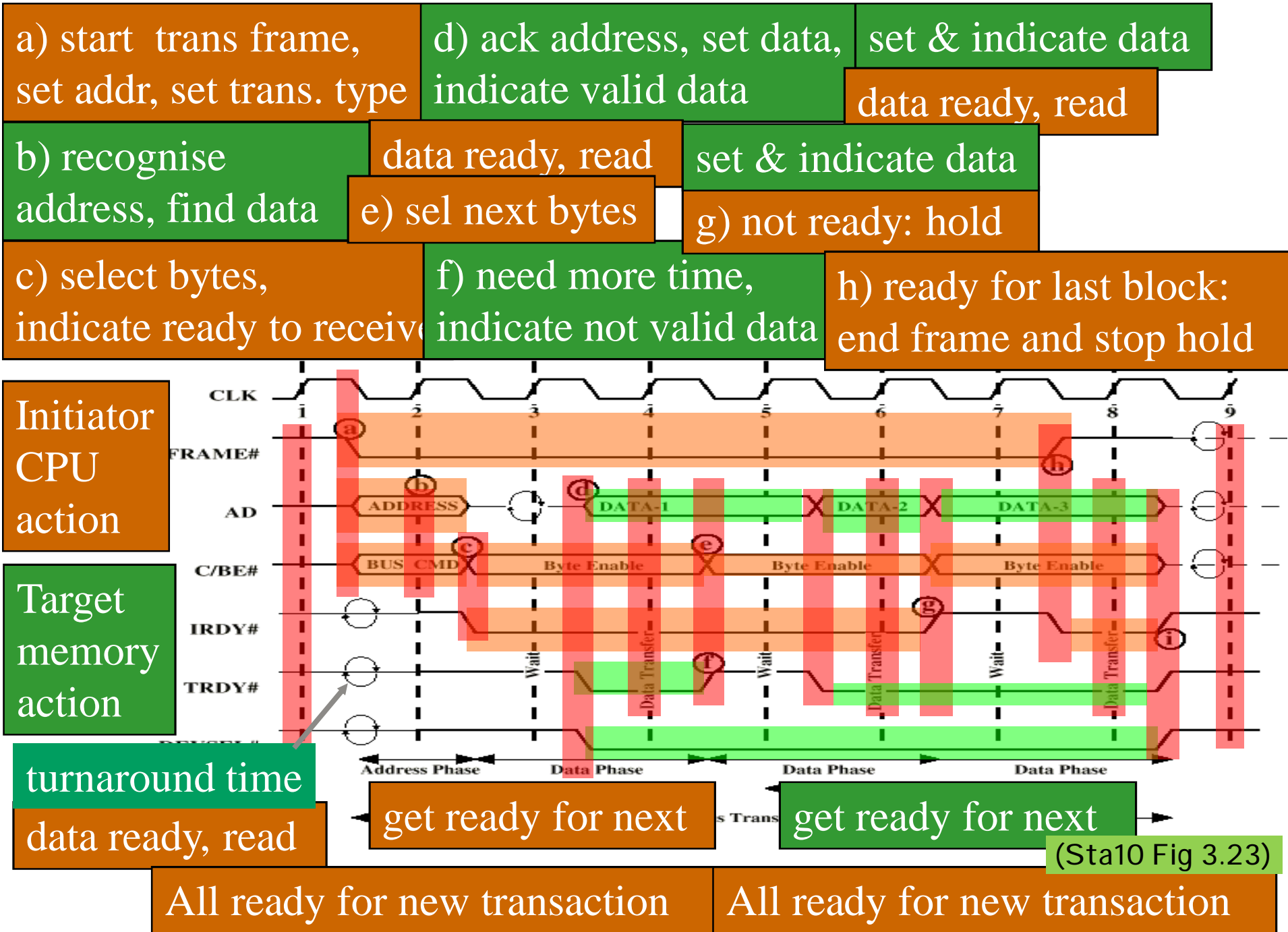



PCI Memory Read

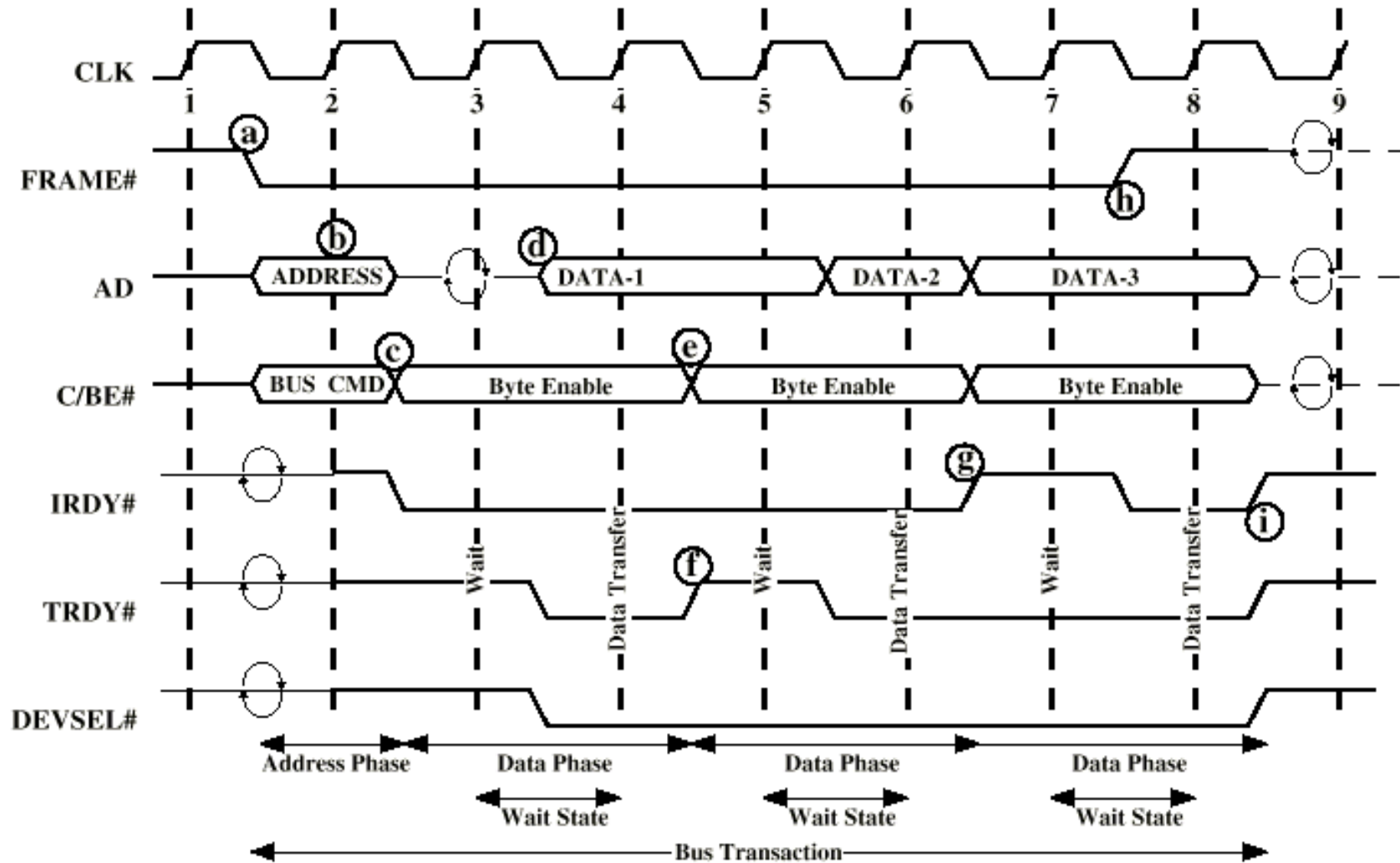

(Sta10 Fig 3.23)

Discussion?



Lecture 2 Summary

- Boolean Algebra → Gates → Circuits
 - Combination circuits, sequential circuits
- Components for CPU design
 - ROM, adder, multiplexer, encoder/decoder
 - flip-flop, register, shift register, counter
- Bus
 - Structure, components, signals, arbitration
 - PCI bus example

Simulations of gates and circuits:

Hades Simulation Framework:

<http://tams-www.informatik.uni-hamburg.de/applets/hades/webdemos/index.html>

<http://tams-www.informatik.uni-hamburg.de/applets/hades/webdemos/16-flipflops/10-srff/srff.html>




Review Questions

- Main differences between synchronous and asynchronous timing?
- Benefits of bus hierarchy?

- Text book review questions
- Text book support page review questions

<http://www.box.net/shared/4597aix1nm>

Simple processor

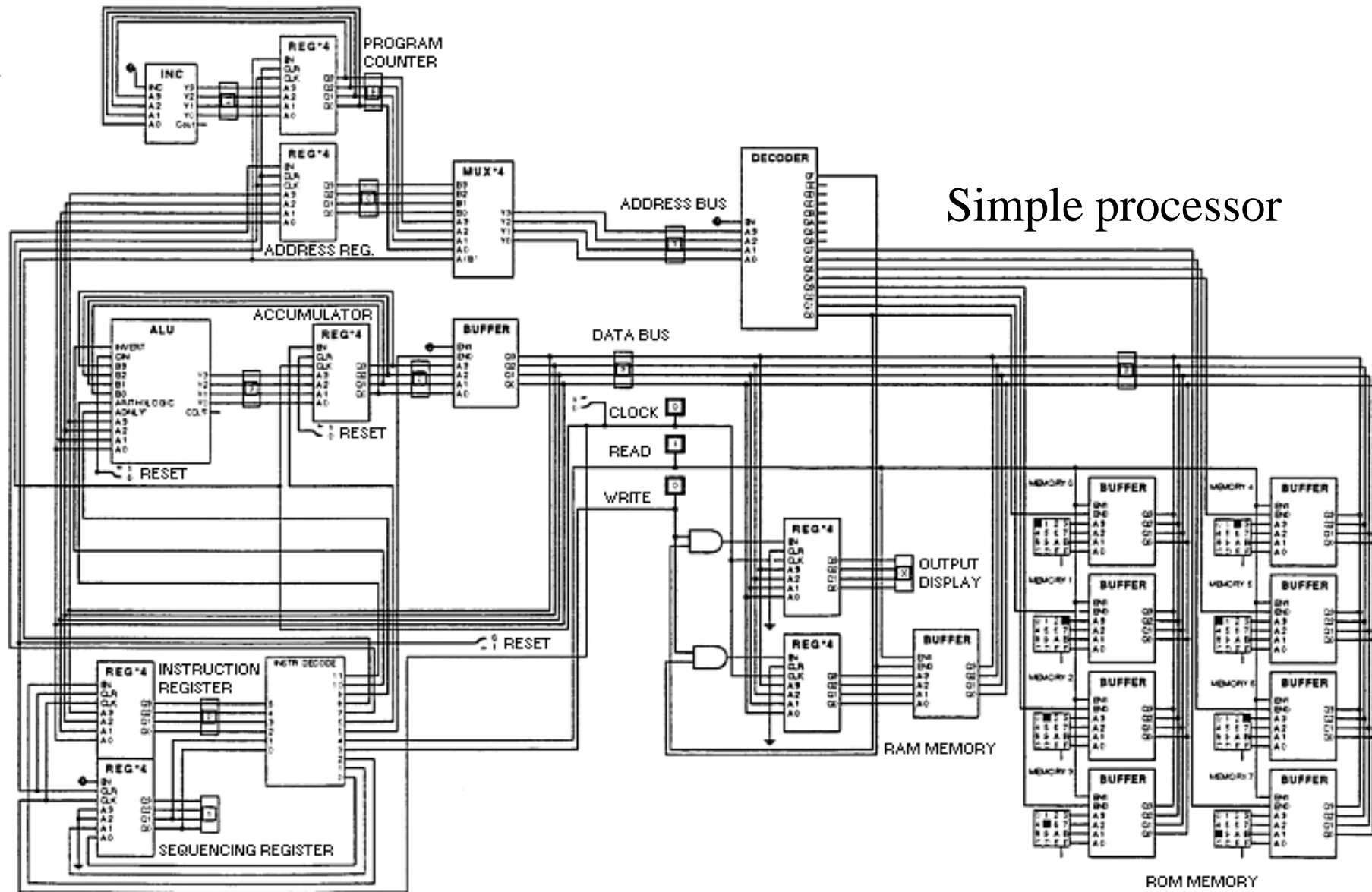

http://www.gamezero.com/team-0/articles/math_magic/micro/stage4.html