



## Digital logic


### Stallings: Appendix B


Boolean Algebra

Combinational Circuits

Simplification


Sequential Circuits

 

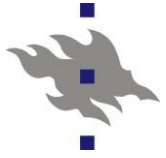

## Computer Organization II

# Boolean Algebra

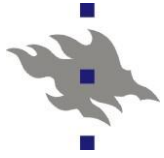

# Boolean Algebra

- George Boole
  - ideas 1854
- Claude Shannon ([kuva](#)) ([gradu](#))
  - apply to circuit design, 1938
  - “father of information theory”



## Topics:

- Describe digital circuitry function
  - programming language?
- Optimise given circuitry
  - use algebra (Boolean algebra) to manipulate (Boolean) expressions into simpler expressions

(piirisuunnittelu)



## Boolean Algebra

- Variables: A, B, C
- Values: TRUE (1), FALSE (0)
- Basic logical operations:
  - binary: AND (  $\cdot$  )
  - binary: OR (  $+$  )
  - unary: NOT (  $\bar{\phantom{A}}$  )
- Composite operations, equations
  - precedence: NOT, AND, OR
  - parenthesis

$$A \bullet B = AB$$

$$B + C$$

$$\bar{A}$$

ja  
tai  
ei

product  
sum  
negation

integer  
arithmetics

$$D = A + \bar{B} \bullet C = A + ((\bar{B})C)$$



## Boolean Algebra

### Other operations

- XOR (exclusive-or)
- NAND
- NOR


$$A \text{ NAND } B = \text{NOT } (A \text{ AND } B) = \overline{AB}$$

$$A \text{ NOR } B = \text{NOT } (A \text{ OR } B) = \overline{A + B}$$

### Truth tables

P	Q	NOT P	P AND Q	P OR Q	P XOR Q	P NAND Q	P NOR Q
0	0	1	0	0	0	1	1
0	1	1	0	1	1	1	0
1	0	0	0	1	1	1	0
1	1	0	1	1	0	0	0

(Sta06 Table B.1)

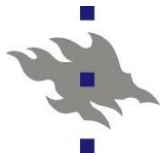

## Postulates and Identities


- How can I manipulate expressions?
  - Simple set of rules?

Basic Postulates		
$A \cdot B = B \cdot A$	$A + B = B + A$	Commutative Laws vaihdantalaki
$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	$A + (B \cdot C) = (A + B) \cdot (A + C)$	Distributive Laws osittelulaki
$1 \cdot A = A$	$0 + A = A$	Identity Elements neutraali-alkiot
$A \cdot \bar{A} = 0$	$A + \bar{A} = 1$	Inverse Elements
Other Identities		
$0 \cdot A = 0$	$1 + A = 1$	alkion ja komplementin tulo ja summa tulo 0'n kanssa, summa 1'n kanssa
$A \cdot A = A$	$A + A = A$	tulo ja summa itsensä kanssa
$A \cdot (B \cdot C) = (A \cdot B) \cdot C$	$A + (B + C) = (A + B) + C$	Associative Laws liitännälait
$\overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A}} + \overline{\overline{B}}$	$\overline{\overline{A} + \overline{B}} = \overline{\overline{A}} \cdot \overline{\overline{B}}$	DeMorgan's Theorem

(Sta06 Table B.2)



## Gates (veräjät / portit)

 

- Implement basic Boolean algebra operations
- Fundamental building blocks
  - 1 or 2 inputs, 1 output
- Combine to build more complex circuits
  - memory, adder, multiplier, ...
- Gate delay
  - change inputs, after gate delay new output available
  - 1 ns? 10 ns? 0.1 ns?

yhteenlaskupiiri,  
kertolaskupiiri

<http://tech-www.informatik.uni-hamburg.de/applets/cmos/cmosdemo.html> (extra material)

Sta06 Fig B.1




## Functionally Complete Set

funktionaalisesti  
täydellinen joukko =>  
joukosta voidaan  
muodostaa kaikki portit

- Can build all basic gates (AND, OR, NOT) from a smaller set of gates
  - With AND, NOT
  - With OR, NOT
  - With NAND alone
  - With NOR alone

(Nämä seuraavat suoraan  
DeMorganin kaavoista )
 
$$A + B = \overline{\overline{A} \cdot \overline{B}}$$



OR with AND and NOT gates

Sta06 Fig B.2, B.3






# Combinational Circuits

yhdistelmäpiirit

Sta06 Fig B.4

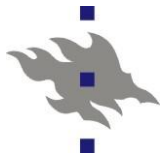- Interconnected set of gates
  - m inputs, n outputs
  - change inputs, wait for gate delays, new outputs
- Each output
  - depends on combination of input signals
  - can be expressed as Boolean function of inputs
  
- Function can be described in three ways
  - with Boolean equations (one equation for each output)
  - with truth table
  - with graphical symbols for gates and wires



## Describing the Circuit

### Boolean equations

$$F = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C}$$


### Truth table

<----- inputs ----->			<- output ->
A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

(Sta06 Table B.3)

### Graphical symbols

Sta06 Fig B.4

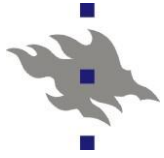

## Computer Organization II

# Simplification

Piirin yksinkertaistaminen

# ■ Simplify Presentation (and Implementation)

## ■ Boolean equations

Sta06 Table B.3

### ■ Sum of products form (SOP)

tulojen summa

Sta06 Fig B.4

$$F = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C}$$

### ■ Product of sums form (POS)

summien tulo

Boolean algebra

$$F = (A + B + C) \cdot (A + B + \overline{C}) \cdot (\overline{A} + B + C) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + \overline{C})$$

Sta06 Fig B.5

## ■ Which presentation is better?

- Fewer gates? Smaller area on chip?
- Smaller circuit delay? Faster?



## Algebraic Simplification

- Circuits become too large to handle?
- Use basic identities to simplify Boolean expressions

$$\begin{aligned} F &= \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} \\ &= \overline{A}B + B\overline{C} = B(\overline{A} + \overline{C}) \end{aligned}$$

Sta06 Fig B.4



Sta06 Fig B.6

- May be difficult to do!
- How to do it automatically?
- Build a program to do it “best”?

$$\begin{aligned} f &= \overline{a}\overline{b}cd + \overline{a}b\overline{c}d + a\overline{b}\overline{c}d + a\overline{b}c\overline{d} \\ &+ ab\overline{c}d + a\overline{b}c\overline{d} + a\overline{b}c\overline{d} + a\overline{b}c\overline{d} \end{aligned}$$



## How so?


$$\begin{aligned}
 F &= \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} \\
 &= \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} \\
 &= (\overline{A}B\overline{C} + \overline{A}BC) + (\overline{A}B\overline{C} + A\overline{B}\overline{C}) \\
 &= \overline{A}B(\overline{C} + C) + (\overline{A} + A)B\overline{C} \\
 &= \overline{A}B(1) + (1)B\overline{C} \\
 &= \overline{A}B + B\overline{C} \\
 &= B(\overline{A} + \overline{C})
 \end{aligned}$$

Boolean algebra:  
 $A+A=A$

And this?


Entäs tämä?
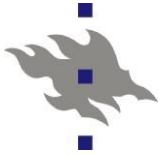
$$\begin{aligned}
 f &= \overline{a}b\overline{c}d + \overline{a}bcd + a\overline{b}\overline{c}d + ab\overline{c}d \\
 &+ abcd + ab\overline{c}d + a\overline{b}cd + a\overline{b}cd
 \end{aligned}$$



 
# Karnaugh Map

- Represent Boolean function (i.e., circuit) truth table in another way
  - Use canonical form: each term has each variable once
  - Use SOP presentation
- Karnaugh map squares
  - Each square is one product (input value combination)
  - Value is one (1) iff the product is present  
o/w value is “empty”



(Sta06 Fig B.7)

(a)  $F = A\bar{B} + \bar{A}B$

 


(b)  $F = \bar{A}B\bar{C} + \bar{A}BC + ABC\bar{C}$


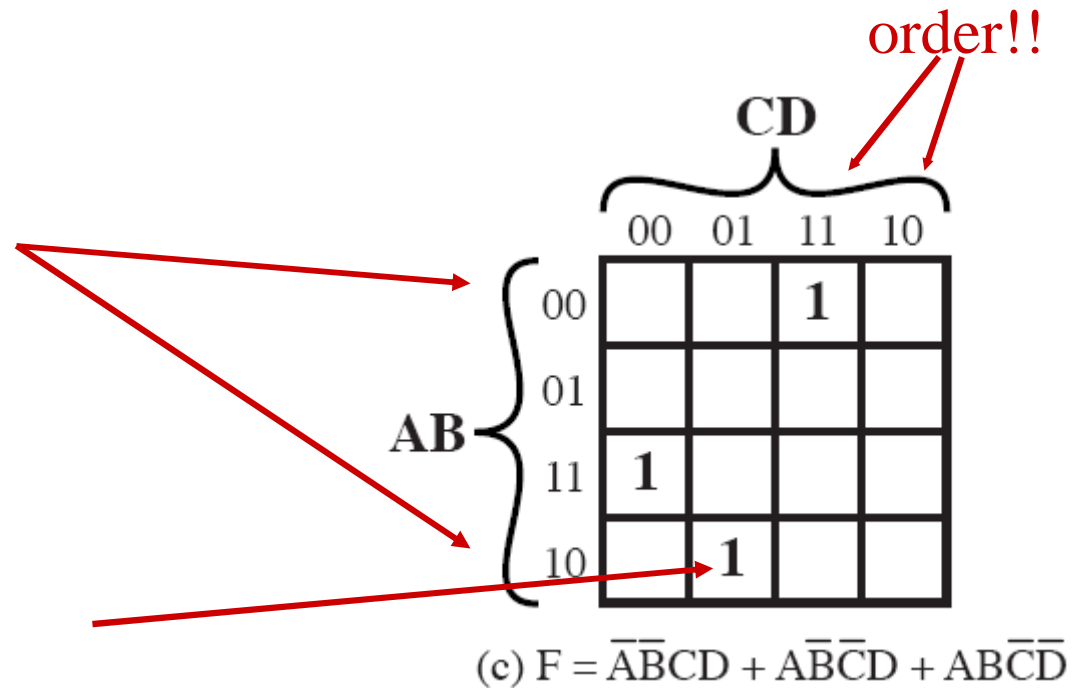
## Karnaugh Map

- Adjacent squares differ only in one input value (wrap around)

- Square for input combination  $\overline{A}\overline{B}CD$  1001




(Sta06 Fig B.7)




 
## Karnaugh Map Simplification

- If adjacent squares have value 1, input values differ only in one variable
- Value of that variable is irrelevant (when all other input variables are fixed for those squares)
- Can ignore that variable for those expressions



$$\begin{aligned}
 & \blacksquare + \bar{A}B\bar{C}D + \bar{A}BCD + \dots \rightarrow \text{ignore } C \quad + \bar{A}BD + \dots
 \end{aligned}$$



# Using Karnaugh Maps to Minimize Boolean Functions (8)

Original function

$$f = \overline{a}b\overline{c}d + \overline{a}bcd + a\overline{b}\overline{c}d + a\overline{b}cd + ab\overline{c}d + abc\overline{d} + abc\overline{d} + abc\overline{d}$$

Canonical form (already OK)

Karnaugh Map


Find smallest number of circles, each with largest number ( $2^i$ ) of 1's


- can wrap-around

Select parameter combinations corresponding to the circles

Get reduced function

$$f = bd + ac + ab$$

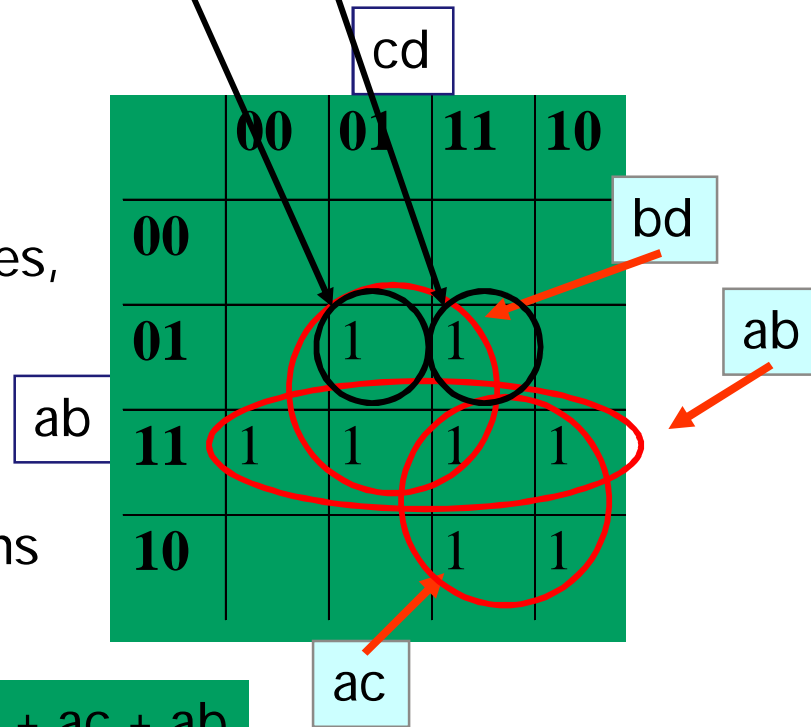


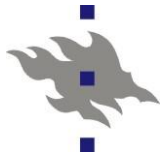


# Impossible Input Variable Combinations

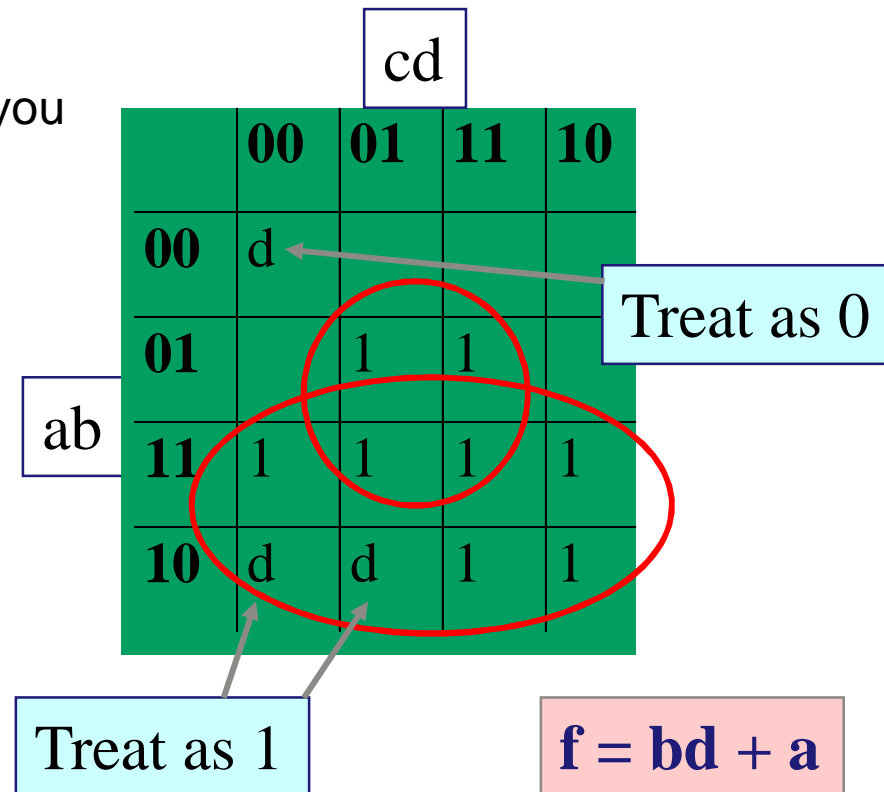(3)


- What if some input combinations can never occur?
  - Mark them "don't care", "d"
  - Treat them as 0 or 1, whichever is best for you
  - More room to optimize



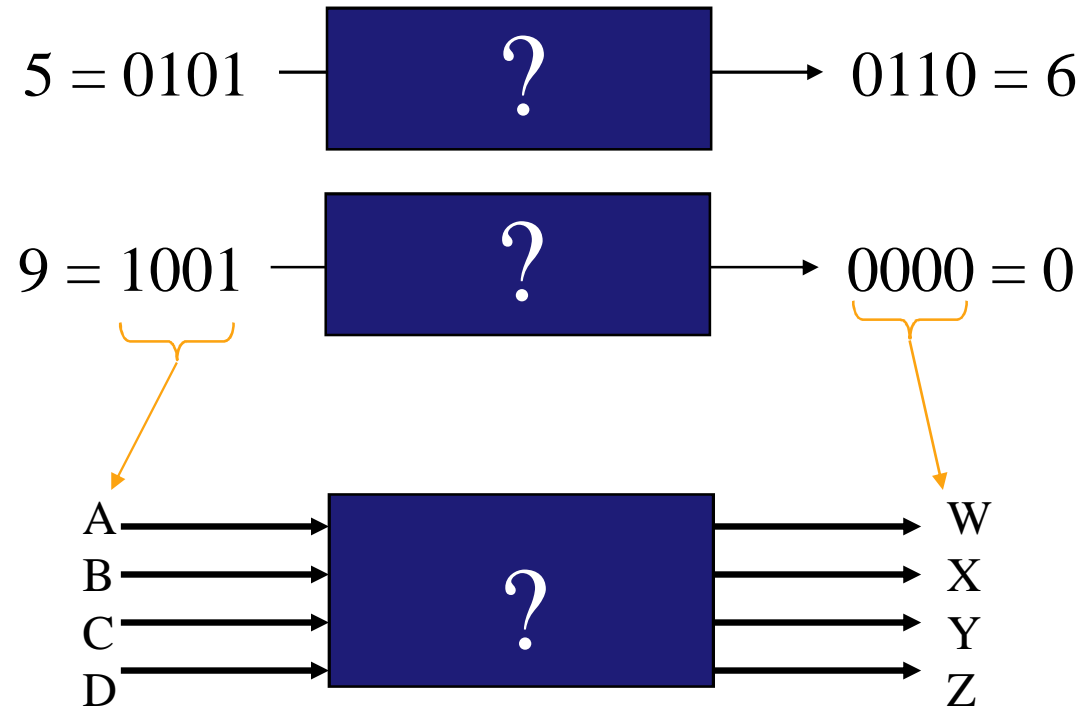- **Example: Circuit to add 1 (mod 10)**
- **to 4-bit BCD decimal number** <sup>(3)</sup>



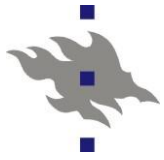- Truth table?
- Karnaugh maps for W, X, Y and Z?




## Example cont.: Truth Table

Truth Table for the One-Digit Packed Decimal Incrementer

Number	Input				Number	Output			
	A	B	C	D		W	X	Y	Z
0	0	0	0	0	1	0	0	0	1
1	0	0	0	1	2	0	0	1	0
2	0	0	1	0	3	0	0	1	1
3	0	0	1	1	4	0	1	0	0
4	0	1	0	0	5	0	1	0	1
5	0	1	0	1	6	0	1	1	0
6	0	1	1	0	7	0	1	1	1
7	0	1	1	1	8	1	0	0	0
8	1	0	0	0	9	1	0	0	1
9	1	0	0	1	0	0	0	0	0
Don't care con- dition	1	0	1	0		d	d	d	d
	1	0	1	1		d	d	d	d
	1	1	0	0		d	d	d	d
	1	1	0	1		d	d	d	d
	1	1	1	0		d	d	d	d
	1	1	1	1		d	d	d	d


No carry!

(Sta06 Table B.4)

 


# Example cont: Karnaugh Map


Sta06 Table B.4

 


(a)  $W = A\bar{D} + \bar{A}BCD$

 

 (b)  $X = B\bar{D} + B\bar{C} + \bar{B}CD$



 (c)  $Y = \bar{A}\bar{C}D + \bar{A}C\bar{D}$



(d)  $Z = \bar{D}$


(Sta06 Fig B.10)


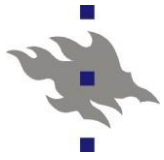
## Other Methods to simplify Boolean expressions

- Why?
  - Karnaugh maps become complex with
    - 6 input variables
- Quine-McKluskey method
  - Tabular method
  - Automatically suitable for programming
- Luque Method
  - Based on dividing circle in different ways
  - Can be fractally expanded to infinitely many variables
- Interesting, but not part of this course
- Details skipped

$\overline{\overline{abcd}}$   
 $\overline{\overline{abcd}}$   
 $\overline{\overline{abcd}}$   
 $\overline{\overline{abcd}}$   
 $\overline{\overline{abcd}}$   
 $\overline{\overline{abcd}}$   
 $\overline{\overline{abcd}}$



## Computer Organization II

# Basic

# Combinatorial Circuits

Building blocks for more complex circuits

- ◆ Multiplexer
- ◆ Encoders/decoder
- ◆ Read-Only-Memory
- ◆ Adder





## Multiplexers

limitin


Sta06 Fig B.12

- Select one of many possible inputs to output

Sta06 Table B.7

- black box
- truth table
- implementation

Sta06 Fig B.13

 

- Each input/output “line” can be many parallel lines

- select one of three 16 bit values
  - $C_{0..15}$  ,  $IR_{0..15}$  ,  $ALU_{0..15}$
- simple extension to one line selection
  - lots of wires, plenty of gates ...

Sta06 Fig B.14

- Used to control signal and data routing

- Example: loading the value of PC



## Encoders/Decoders

- Exactly one of many Encoder input or Decoder output lines is 1
- Encode that line number as output
  - hopefully less pins (wires) needed this way
  - optimise for space, not for time
  - Example:
    - encode 8 input wires with 3 output pins
    - route 3 wires around the board
    - decode 3 wires back to 8 wires at target

space-time tradeoff

Sta06 Fig B.15

Ex. Choosing the right memory chip from the address bits.





## Read-Only-Memory (ROM) (5)

- Given input values, get output value
  - Like multiplexer, but with **fixed data**
- Consider input as address, output as contents of memory location

- Example

- Truth tables for a ROM **Sta06 Table B.8**

- 64 bit ROM
    - 16 words, each 4 bits wide

Mem (7) = 4

Mem (11) = 14


- Implementation with decoder & or gates

**Sta06 Fig B.20**




## Adders

- 1-bit adder

 

- 1-bit adder with carry

 


- Implementation

Sta06 Table B.9, Fig B.22

Compare to ROM?

- Build a 4-bit adder from four 1-bit adders

Sta06 Fig B.21

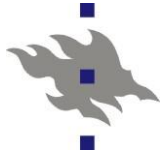

## Computer Organization II

# Sequential Circuits


sarjalliset  
piirit

- ◆ Flip-Flop
- ◆ S-R Latch
- ◆ Registers
- ◆ Counters




 
## Sequential Circuit (sarjallinen piiri)

- Circuit has (modifiable) internal state
  - remembers its previous state
- Output of circuit depends (also) on internal state
  - not only from current inputs
  - $\text{output} = f_o(\text{input}, \text{state})$
  - $\text{new state} = f_s(\text{input}, \text{state})$
- Circuits needed for
  - processor control
  - registers
  - memory



 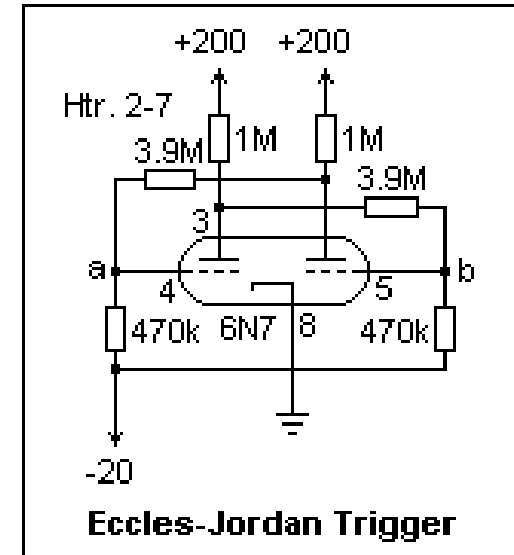
## Flip-Flop (kiikku)

- William Eccles & F.W. Jordan
  - with vacuum tubes, 1919
- 2 states for Q (0 or 1, true or false)
- 2 outputs
  - complement values
  - both always available on different pins
- Need to be able to change the state (Q)






## S-R Flip-Flop or S-R Latch (salpa)

 

S = “SET” = “Write 1” = “set S=1 for a short time”

R = “RESET” = “Write 0” = “set R=1 for a short time”

 nor (0, 0) = 1  
nor (0, 1) = 0  
nor (1, 0) = 0  
nor (1, 1) = 0









## S-R Latch Stable States (4)

- 1 bit memory (value = value of Q)
- bistable, when R=S=0
  - Q=0?
  - Q=1?

nor (0, 0) = 1  
nor (0, 1) = 0  
nor (1, 0) = 0  
nor (1, 1) = 0

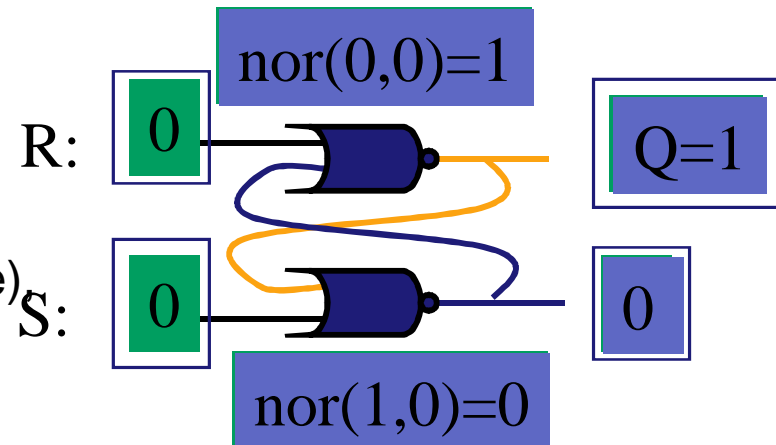
$t = f_o(\text{input, state})$   
 $S = f_s(\text{input, state})$



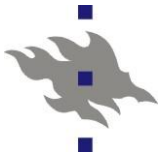


## S-R Latch Set (=1) and Reset (=0) (17)


Write 1:  $S = 0 \rightarrow 1 \rightarrow 0$

 

Write 0:  $R = 0 \rightarrow 1 \rightarrow 0$

 nor (0, 0) = 1  
nor (0, 1) = 0  
nor (1, 0) = 0  
nor (1, 1) = 0




 

## Clocked Flip-Flops

- State change can happen only when clock is 1
  - more control on state changes

- Clocked S-R Flip-Flop

 

- D Flip-Flop Sta06 Fig B.27

(Sta06 Fig B.26)

- only one input D
  - D = 1 and CLOCK → write 1
  - D = 0 and CLOCK → write 0

- J-K Flip-Flop Sta06 Fig B.28

- Toggle Q when J=K=1


Sta06 Fig B.29



## Registers

- Parallel registers
  - read/write
  - CPU user registers
  - additional internal registers
  
- Shift Registers
  - shifts data 1 bit to the right
  - serial to parallel?
  - ALU ops?
  - rotate?

Sta06 Fig B.30

 

(Sta06 Fig B.31)




## Counters

- Add 1 to stored counter value
- Counter
  - parallel register plus increment circuits
- Ripple counter (aalto, viive)
  - asynchronous
  - increment least significant bit,
  - and handle “carry” bit as far as needed
- Synchronous counter
  - modify all counter flip-flops simultaneously
  - faster, more complex, more expensive

space-time tradeoff

Sta06 Fig B.32

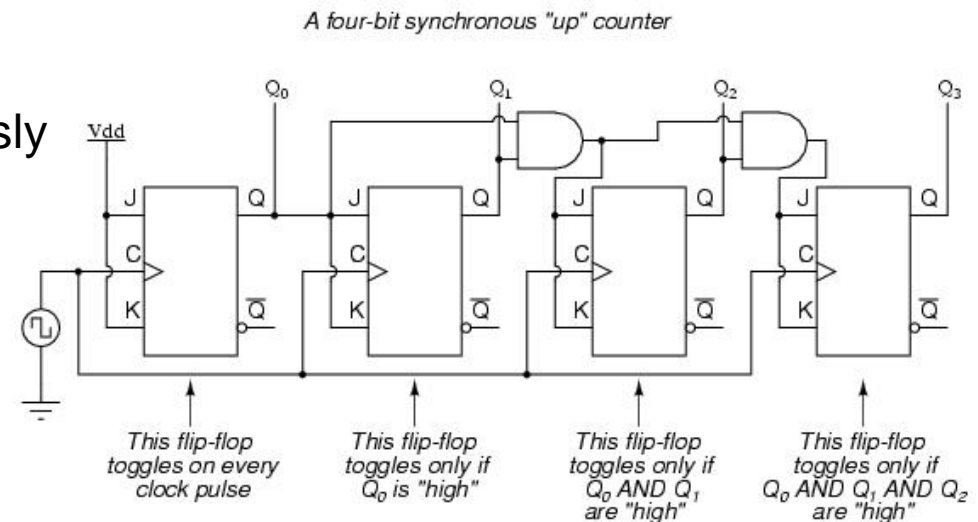

(<http://www.allaboutcircuits.com>)




## Summary

- Boolean Algebra → Gates → Circuits
  - can implement all with NANDs or NORs
  - simplify circuits:
    - Karnaugh, (Quine-McKluskey, Luque, ...)
  
- Components for CPU design
  - ROM, adder
  - multiplexer, encoder/decoder
  - flip-flop, register, shift register, counter


Simulations of gates and circuits:

 Hades Simulation Framework: <http://tams-www.informatik.uni-hamburg.de/applets/hades/webdemos/index.html>



# -- End of Appendix B: Digital Logic --

## Simple processor

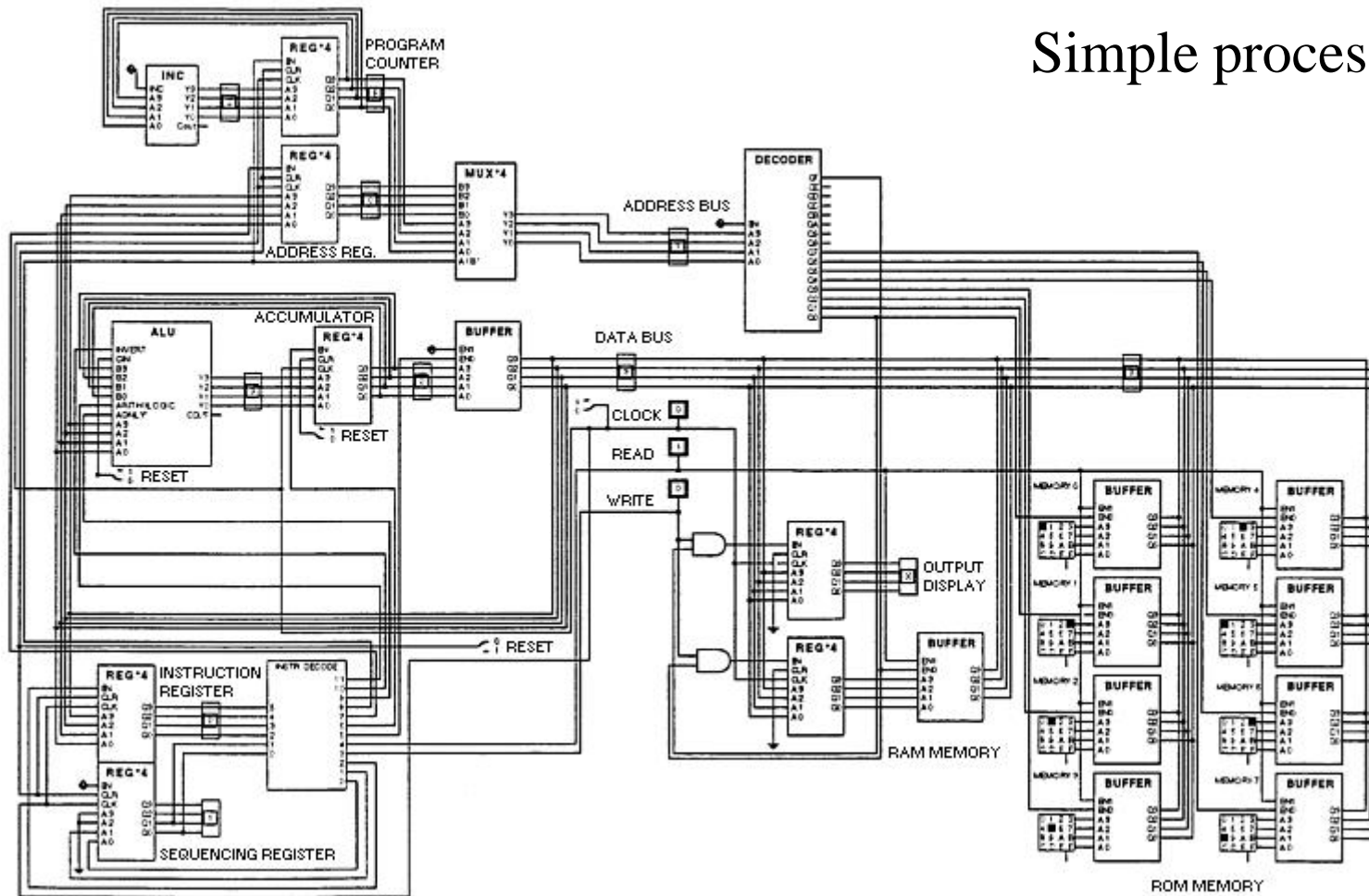

[http://www.gamezero.com/team-0/articles/math\\_magic/micro/stage4.html](http://www.gamezero.com/team-0/articles/math_magic/micro/stage4.html)



## Kertauskysymyksiä/Review questions

- DeMorganin laki?
- Miten boolean funktio minimoidaan Karnaugh- kartan avulla?
- Mitä eroa sarjallisessa piirissä on verrattuna ”normaaliin” kombinatoriseen piiriin?
- Miten S-R kiikku toimii?

- DeMorgan's theorem?
- How to minimize a Boolean function using Karnaugh's map?
- How do sequential circuits differ from 'normal' combinational circuits?
- How does the S-R flip-flop function?